

2 0 2 2

( February )

ELECTRONICS

( Elective/Honours )

( **Feedback and Oscillator, Multivibrator,  
Operational amplifier, Digital Electronics—I** )

[ ELEC-301 (T) ]

Marks : 56

Time : 3 hours

*The figures in the margin indicate full marks  
for the questions*

Answer **one** question from each Unit

UNIT—I

1. (a) Draw a neat block diagram showing feedback action of an amplifier.
- (b) Deduce the relation between voltage gain with feedback  $A_{vf}$  and voltage gain without feedback  $A_v$  and mention the conditions for negative and positive feedback.

- (c) Mention the important properties of negative feedback (without deduction).
- (d) Discuss in brief with suitable diagram, amplitude distortion.
- (e) Discuss in brief with suitable diagram, frequency distortion in an amplifier.

3+3+2+3+3

2. (a) Draw a block diagram showing the essential parts of an oscillator circuit.
- (b) What are the two basic requirements which need to be satisfied for a circuit to oscillate?
- (c) Discuss in brief the working of a basic L-C tank circuit as an oscillator and mention the problem faced if one uses it as an oscillator.
- (d) Discuss in brief with suitable diagram, a Wien bridge oscillator.

2+2+5+5

UNIT—II

3. (a) Mention a few uses of a multivibrator.
- (b) Draw the circuit diagram of astable multivibrator using transistor. Explain with necessary timing diagram, the working of astable multivibrator using transistor.

( 3 )

- (c) Discuss with a neat circuit diagram, the working of bistable multivibrator.
- (d) Determine the time period and frequency of oscillation for an astable multivibrator with the following component values :

$$R_1 = 2k, R_L = 10k, C_1 = 0.01F, \\ C_2 = 0.1F \quad 1+6+4+3$$

4. (a) Draw the pin diagram of IC 555 timer with proper labelling.
- (b) Discuss with necessary circuit diagram, the working of a monostable multivibrator with IC 555 timer.
- (c) Draw the circuit diagram of astable multivibrator using OP-AMP. Discuss with necessary timing diagram how the output voltage level is shifted. 2+6+6

UNIT—III

5. (a) Discuss the working of a differential amplifier.
- (b) Derive the expression of voltage gain of a non-inverting amplifier. 7+7
6. (a) Derive an expression for voltage gain of an active low-pass filter designed with an OP-AMP.

22D/170

( Turn Over )

( 4 )

- (b) What is a virtual ground?
- (c) A differential amplifier has differential gain and common-mode gain of 150 and 0.5 respectively. Find the CMRR in dB.
- (d) Derive an expression for output of an integrator circuit designed with an OP-AMP. 6+2+2+4

UNIT—IV

7. (a) Convert the following binary numbers into their decimal equivalent :
- (i) 0.01
- (ii) 1.01
- (b) Convert the following decimal numbers into their binary equivalent :
- (i) 4.25
- (ii) 0.562
- (c) Convert the following octal numbers into their hex equivalent :
- (i)  $(305)_8$
- (ii)  $(0.47)_8$
- (d) Represent the following decimal numbers in 1's complement form :
- (i) 15
- (ii) 31

22D/170

( Continued )

(e) Find 2's complement of the following numbers :

(i)  $(11011)_2$

(ii)  $(10001)_2$

(f) Add the following two numbers using 2's complement method :

$$\begin{array}{r} -27 \\ \underline{\phantom{-}35} \\ \text{Add} = \end{array} \qquad 2+2+2+2+2+4$$

8. (a) Simplify the following three-variable expression using Boolean algebra :

$$Y(A, B, C) \quad m(0, 2, 4, 6)$$

(b) Minimize the following expression using K-map :

$$Y(A, B, C) \quad m(0, 1, 3, 5)$$

(c) Convert the following Boolean function into the standard POS form and express in max-terms :

$$Y(A, B, C) (A \ B)(B \ C)(A \ \bar{B} \ \bar{C})$$

(d) Write down the truth table of a three-input EXOR gate and EXNOR gate. Also using basic gates, draw the circuit for an EXOR gate. 3+3+5+3

★ ★ ★